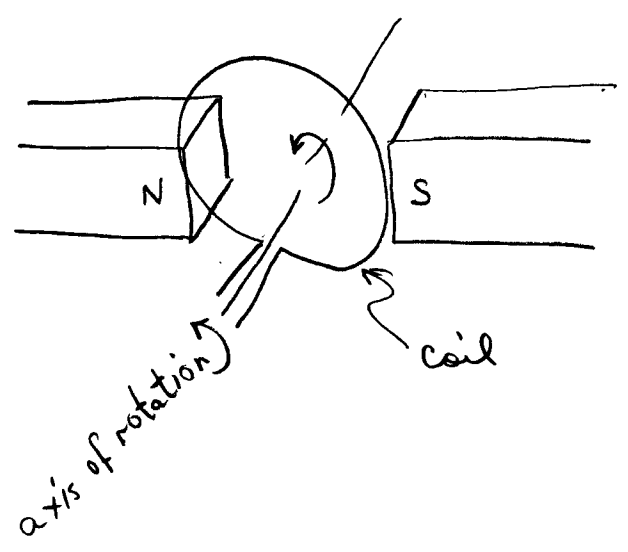


Chapter 33 Alternating Current Circuits

33.1 AC Sources and Phasors



When a coil is rotated in a magnetic field, an EMF is induced proportional to the change in the number of B field lines crossing through the loop.
 (see Chapter 32 for details)

Thus, a coil rotating at an angular frequency, ω rad/s, generates a voltage $V = V_{max} \sin \omega t$

where $\omega = 2\pi f \leftarrow f = \text{frequency, cycles/s}$
 $= \frac{2\pi}{T} \leftarrow T = \text{period, s.}$

In North America, $f = 60 \text{ cycles/s} = 60 \text{ Hz (Hertz)}$

$\therefore \omega = 2\pi \times 60 = 377 \text{ rad/s.}$

This chapter uses phasor diagrams to investigate ac circuit behaviour involving:

- resistors (R)
- inductors (L)
- capacitors (C)

Applications: household and industrial wiring.

33.2 Resistors in an AC Circuit

From Kirchhoff's loop equation:

$$\sum \Delta V = 0$$

$$\therefore V - V_R = 0$$

$$\therefore V = V_R = V_{\max} \sin \omega t = \text{instantaneous voltage drop across } R$$

$$\therefore i_R = \frac{V}{R} = \frac{V_{\max}}{R} \sin \omega t = I_{\max} \sin \omega t$$

Thus i_R is in phase with V_R


Notes:

Average of i_R or $V_R = 0$

Power dissipated in the resistor:

$$P = i^2 R$$
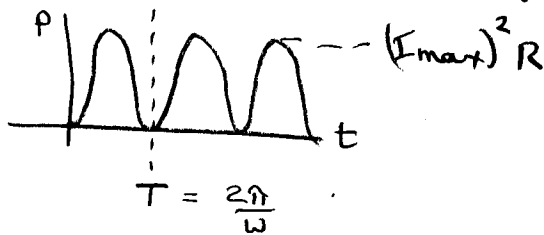
$$P_{\text{average}} = \int_0^T P(t) dt = (i^2)_{\text{average}} R$$






$$R I_{\max}^2 \int_0^T \sin^2 \omega t dt = \frac{I_{\max}^2 R}{2}$$

$$I_{\text{rms}} = \sqrt{\frac{I_{\max}^2}{2}} = \frac{1}{\sqrt{2}} I_{\max} = 0.707 I_{\max}$$

↑
root mean square
 $\equiv \sqrt{\text{average}(i^2)}$

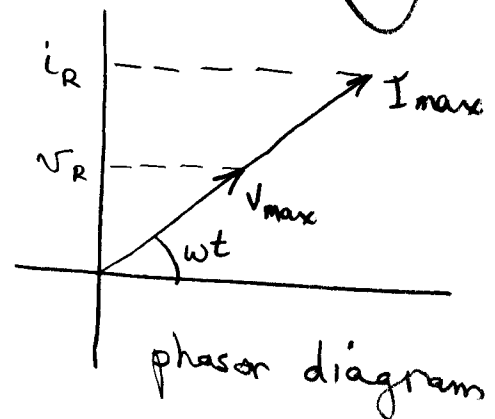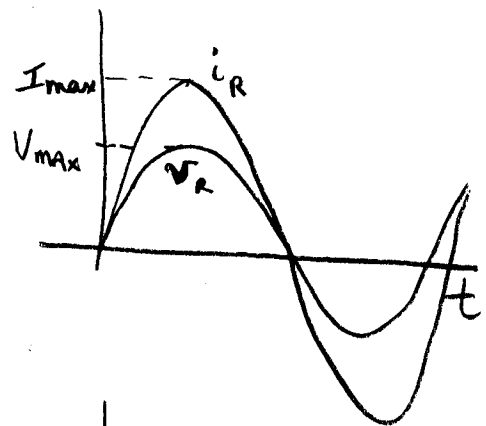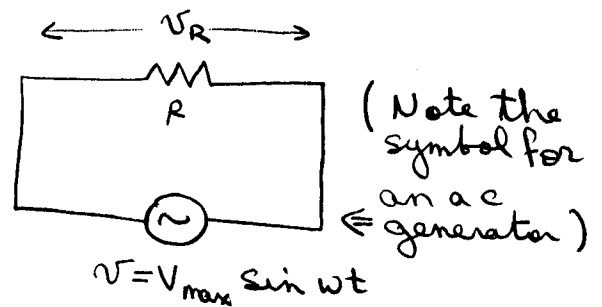Note: DC power at current I_{rms} is same as AC power with current $I_{\max} \sin(\omega t)$



Similarly, $V_{rms} = \frac{V_{max}}{\sqrt{2}} = 0.707 V_{max}$

The 120 V household current is really a V_{rms} of 120 V.

Thus $V_{max} = \frac{120}{0.707} = 170 \text{ V.}$


Multimeters typically display rms values.

Example rms Current

Find V_{rms} , I_{rms}

$$V_{rms} = \frac{V_{max}}{\sqrt{2}} = \frac{200}{\sqrt{2}} = \underline{141 \text{ V}}$$
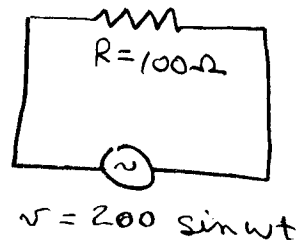
$$I_{rms} = \frac{V_{rms}}{R} = \frac{141 \text{ V}}{100 \Omega} = \underline{1.41 \text{ A}}$$




33.3 Inductors in an AC Circuit

Using Kirchhoff again:



$$V_L - L \frac{di}{dt} = 0$$

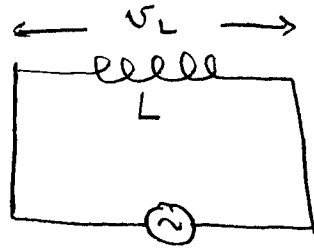or $L \frac{di}{dt} = V_{\max} \sin \omega t$



Integrating, $i_L = -\frac{V_{\max}}{\omega L} \cos \omega t = \frac{V_{\max}}{\omega L} \sin(\omega t - \pi/2)$

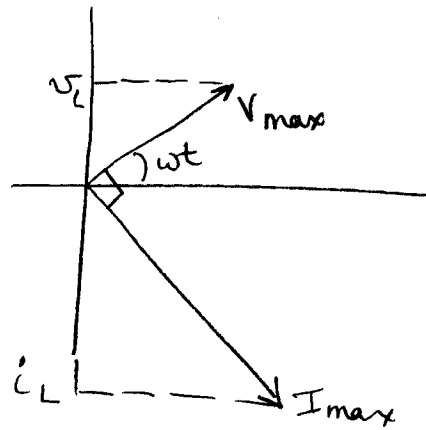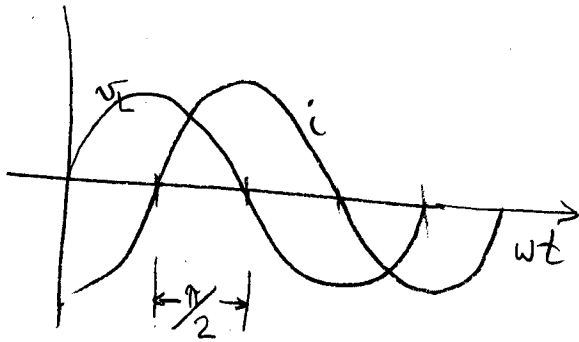ie current in an inductor lags voltage by 90° .



Define inductive reactance:

$$X_L = \omega L$$

$$\therefore I_{\max} = \frac{V_{\max}}{\omega L} = \frac{V_{\max}}{X_L}$$

$X_L \sim$ units of Ω .
 \sim to resistor

$X_L \uparrow$ as $\omega \uparrow$


Makes physical sense - inductors have "inertia" like mass.

Example a Purely Inductive AC Circuit

Find X_L and I_{rms} .

$$X_L = \omega L = (2\pi \times 60) \text{ s}^{-1} (0.025) \text{ H} \\ = \underline{9.42 \ \Omega}$$
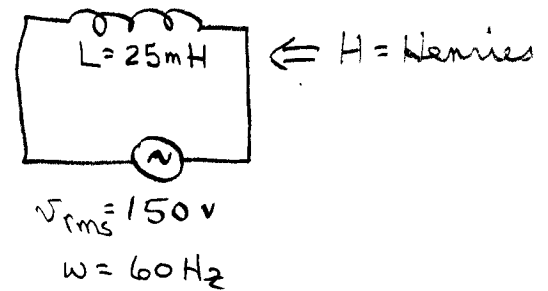
$$I_{rms} = \frac{V_{rms}}{X_L} = \frac{150}{9.42} = \underline{15.9 \text{ A}}$$



33.4 Capacitors in an AC Circuit

$$V - V_c = 0$$

$$\therefore V = V_c = V_{\max} \sin \omega t$$

$$\text{But } V_c = \frac{Q}{C}$$

$$\therefore Q = CV_{\max} \sin \omega t$$

$$\therefore i = \frac{dQ}{dt} = \omega C V_{\max} \cos \omega t = \omega C V_{\max} \sin(\omega t + \frac{\pi}{2})$$

Thus current leads voltage in a capacitor.

Define capacitive reactance:



$$X_c = \frac{1}{\omega C}$$

$$\therefore I_{\max} = \frac{V_{\max}}{X_c} \leftarrow \text{units of } \Omega.$$

~ to resistance.

$$X_c \uparrow \text{ as } \omega \downarrow$$

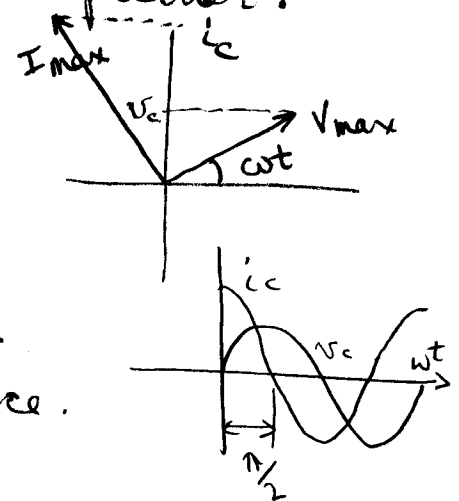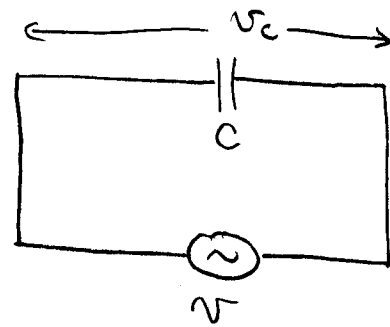Makes physical sense - capacitor acts like a storage unit. Tends to an open circuit as you approach dc ($\omega = 0, X_c = \infty \Rightarrow I_{\max} = 0$).




Example: A Purely Capacitive AC Circuit

Find X_c , I_{rms} .

$$X_c = \frac{1}{\omega C} = \frac{1}{(2\pi \times 60)(8 \times 10^{-6})} \Omega$$

$$= \underline{332 \Omega}$$
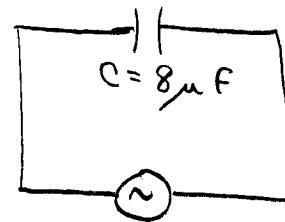
$$I_{rms} = \frac{150}{332} = \underline{0.452 \text{ A}}$$



$$V_{rms} = 150 \text{ V}$$


$$\omega = 60 \text{ Hz}$$

33.5 The RLC Series Circuit


Let us assume that

$$i = I_{\max} \sin(\omega t - \phi)$$

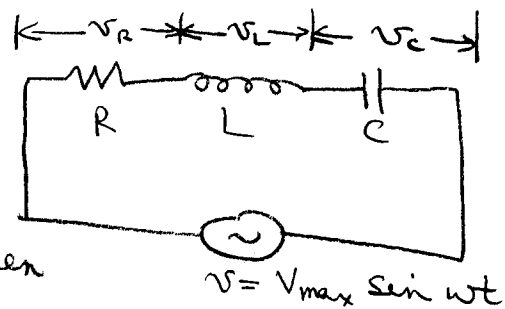where ϕ is the phase angle between i + v .



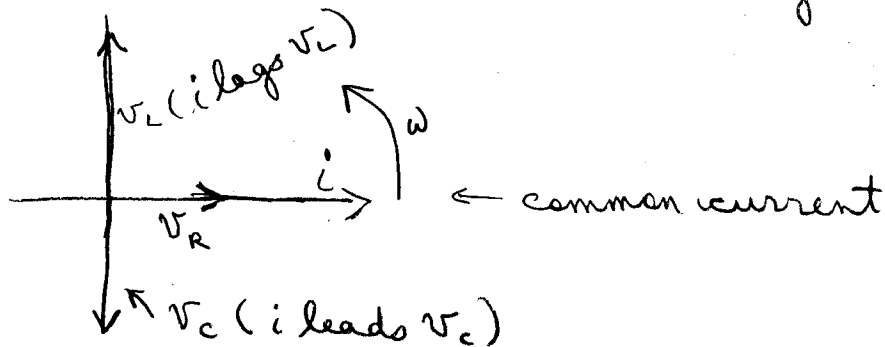The current is continuous + the same everywhere in the loop. The component voltages are as shown:




$$\therefore v = v_R + v_L + v_C$$

$$= I_{\max} R \sin \omega t + I_{\max} X_L \sin(\omega t + \pi/2) + I_{\max} X_C \sin(\omega t - \pi/2)$$

$$= V_R \sin \omega t + V_L \sin(\omega t + \pi/2) + V_C \sin(\omega t - \pi/2)$$

Take a vector sum:

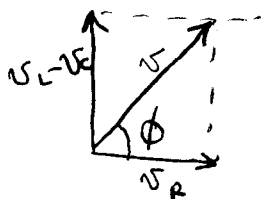

$$\therefore V_{\max} = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$= I_{\max} \sqrt{R^2 + (X_L - X_C)^2}$$

$$\equiv I_{\max} Z$$

↑ impedance

$$\tan \phi = \frac{X_L - X_C}{X_R}$$

Example: Analyzing a Series RLC Circuit

Find Z , ϕ , V_R , V_L , V_C

$$\omega = 2\pi f = 377 \text{ sec}^{-1}$$


$$\therefore X_L = \omega L = 226 \Omega$$

$$+ X_C = \frac{1}{\omega C} = 758 \Omega$$

$$\therefore Z = \sqrt{250^2 + (226 - 758)^2}$$

$$= 588 \Omega$$
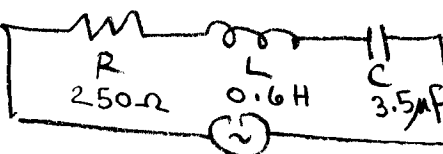
$$I_{\max} = \frac{V_{\max}}{Z} = \frac{150}{588} = 0.255 \text{ A}$$



$$v = 150 \sin \omega t$$

$$f = 60 \text{ Hz}$$

$$\begin{aligned} V_R &= I_{\max} R = 0.255 \times 250 \\ &= 63.8 \text{ V} \\ V_L &= I_{\max} X_L = 57.6 \text{ V} \\ V_C &= I_{\max} X_C = 193 \text{ V} \end{aligned}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{X_R} \right) = \tan^{-1} \left(\frac{226 - 758}{250} \right) = -64.8^\circ$$


ie $\phi < 0$, \therefore current leads the voltage
(more capacitance than inductance)

$$\therefore v = 63.8 \sin 377t + 57.6 \cos 377t - 193 \cos 377t$$

Example: Finding L from a Phase Diagram

Given $R = 800 \Omega$, $C = 4 \mu\text{F}$, $f = 60 \text{ Hz}$, v_c lags v by 30°

Find L in a series RLC circuit.

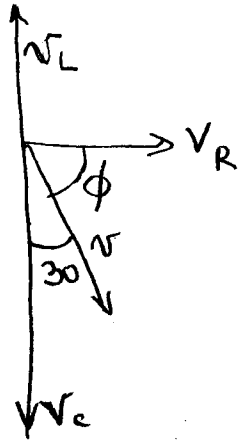

We have: $\tan \phi = \frac{X_L - X_C}{X_R}$

$\therefore X_L = X_C + X_R \tan \phi$

$X_C = \frac{1}{377 \times 4 \times 10^{-6}} \Omega = 663.1 \Omega$

$X_R = 800 \Omega$

$\tan \phi = \tan 60^\circ = 1.732$

$\therefore X_L = 2048 \Omega \Rightarrow L = \frac{X_L}{\omega} = \underline{\underline{5.44 \text{ H}}}$


33.6 Power in an AC Circuit

Instantaneous power in an inductor = $i_L v_L$

$$= \frac{V_{\max}}{\omega L} \sin(\omega t - \pi/2) V_{\max} \sin \omega t = -\frac{V_{\max}^2}{\omega L} \sin \omega t \cos \omega t$$

Starting from $t=0$, the instantaneous power, $i_L v_L$, changes sign every $1/4$ cycle (i.e. every $\pi/2$). Thus, the

maximum stored energy is

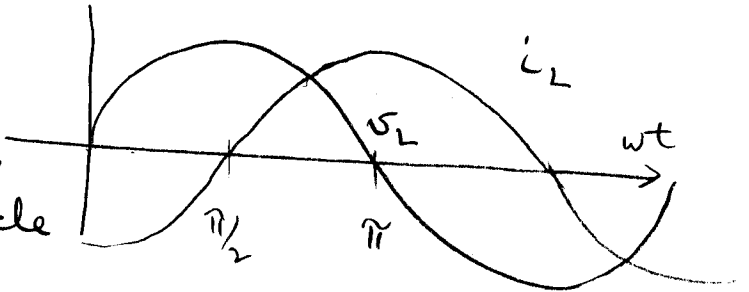

$$\int_{\pi/2\omega}^{\pi/\omega} i_L(t) v_L(t) dt = \frac{1}{\omega} \int_{\pi/2}^{\pi} i_L(\theta) v_L(\theta) d\theta \quad (\theta = \omega t)$$


$$= -\frac{V_{\max}^2}{\omega L} \int_{\pi/2}^{\pi} \sin \theta \cos \theta d\theta = -\frac{V_{\max}^2}{\omega L} \int_{\pi/2}^{\pi} \sin \theta d(\sin \theta)$$

$$= -\frac{V_{\max}^2}{\omega L} \left[\frac{\sin^2 \theta}{2} \right]_{\pi/2}^{\pi} = +\frac{V_{\max}^2}{2\omega L} = \frac{1}{2\omega} I_{\max} V_{\max}$$

$$= \frac{1}{2} L I_{\max}^2 \quad \text{since} \quad V_{\max} = I_{\max} \omega L$$

But this energy is given up to the circuit on the next $1/4$ cycle. Thus, energy is not dissipated in an inductor.
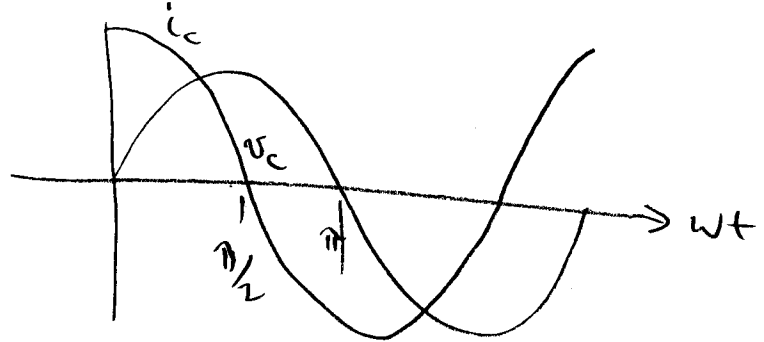
$$\begin{aligned}
 \text{Instantaneous power in a capacitor} &= i_c v_c \\
 &= V_{\max} \cdot \omega C \cdot \sin(\omega t + \pi/2) V_{\max} \sin \omega t \\
 &= V_{\max}^2 \omega C \sin \omega t \cos \omega t
 \end{aligned}$$



As per the inductor, the stored energy is

$$\begin{aligned}
 \int_0^{\pi/2\omega} i_c(t) v_c(t) dt &= \frac{1}{\omega} \int_0^{\pi/2} i_c(\theta) v_c(\theta) d\theta \\
 &= V_{\max}^2 \cdot \frac{\omega C}{\omega} \int_0^{\pi/2} \sin \theta \cos \theta d\theta \\
 &= \frac{C V_{\max}^2}{2}
 \end{aligned}$$


Again, this energy is given up on the next $\frac{1}{4}$ cycle. Thus, energy is not dissipated in a capacitor.

Instantaneous power in a resistor = $i_R V_R$

$$= \frac{V_{\max}}{R} \sin \omega t \cdot V_{\max} \sin \omega t$$

$$= \frac{V_{\max}^2}{R} \sin^2 \omega t$$

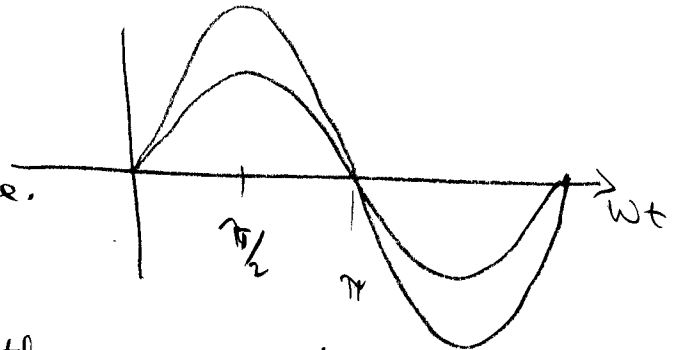Note that power is always +ve.
(ie energy is dissipated)



In one complete cycle, the energy dissipated is

$$\int_0^{2\pi/\omega} i_R(t) V_R(t) dt = \frac{V_{\max}^2}{\omega R} \int_0^{2\pi} \sin^2 \omega t \, d(\omega t)$$

$$= \frac{V_{\max}^2}{\omega R} \cdot \pi$$

$$\left[\text{Note } \int \sin^2 x \, dx = \frac{1}{2}x - \frac{1}{4}\sin 2x \right]$$

The time for 1 cycle is $T = \frac{2\pi}{\omega}$

∴ The average power is $\left(\frac{V_{\max}^2 \cdot \pi}{\omega R} \right) / T$

$$= \frac{1}{2} \frac{V_{\max}^2}{R} = \frac{1}{2} I_{\max}^2 R$$

Power in a RLC series circuit is, in general:

$$P(t) = i(t)v(t) = I_{\max} \sin(\omega t - \phi) V_{\max} \sin \omega t$$

$$= I_{\max} V_{\max} \sin \omega t \sin(\omega t - \phi)$$

Using the trig identity $\sin(a \pm b) = \sin a \cos b \pm \cos a \sin b$,

$$P(t) = I_{\max} V_{\max} \sin^2 \omega t \cos \phi - I_{\max} V_{\max} \sin \omega t \cos \omega t \cos \phi$$

Integrating over 1 cycle:

$$P_{\text{average}} = \frac{1}{T} \int_0^T P(t) dt = \frac{1}{(2\pi/\omega)} \cdot \left(\frac{1}{\omega}\right) \int_0^{2\pi} P(\theta) d\theta$$

$$= \frac{1}{2\pi} \int_0^{2\pi} P(\theta) d\theta = \frac{I_{\max} V_{\max} \cos \phi}{2\pi} \left[\int_0^{2\pi} \sin^2 \theta d\theta - \int_0^{2\pi} \sin \theta \cos \theta d\theta \right]$$

$$= \frac{I_{\max} V_{\max} \cos \phi}{2\pi} [\pi - 0] = \frac{I_{\max} V_{\max} \cos \phi}{2}$$

$$= I_{\text{rms}} V_{\text{rms}} \cos \phi$$

this is called the power factor


Note that since $\cos \phi = \frac{V_R}{V_{\max}} = \frac{I_{\max} R}{V_{\max}}$ we have:

$$P_{\text{average}} = \frac{I_{\max} V_{\max}}{2} \cdot \frac{I_{\max} R}{V_{\max}} = \frac{I_{\max}^2 R}{2} = I_{\text{rms}}^2 R$$

This is just what we found for the power dissipated in the resistor. Thus we are consistent.

Example: Average Power in a RLC Series Circuit

Find P_{average} .

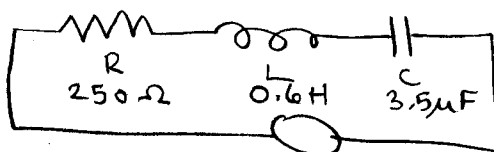

$$v = 150 \sin \omega t$$

$$f = 60 \text{ Hz}$$

$$V_{\text{rms}} = \frac{V_{\text{max}}}{\sqrt{2}} = \frac{150}{\sqrt{2}} = 106 \text{ V}$$

$$I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}} = \frac{V_{\text{max}}/Z}{\sqrt{2}} = \frac{0.255 \text{ A}}{\sqrt{2}} = 0.180 \text{ A}$$

see example in 33.5 for calculation

$$\phi = -64.8^\circ$$

$$\therefore P_{\text{average}} = I_{\text{rms}} V_{\text{rms}} \cos \phi = 0.180 \times 106 \times 0.426$$

$$= 8.13 \text{ W}$$

compare to P_{average} of resistor: $I_{\text{rms}}^2 R = (0.180)^2 \times 250 \text{ W}$

$$= 8.13 \text{ W.}$$

33.7 Resonance in a Series RLC Circuit

From 33.5 we found:

$$I_{\max} = \frac{V_{\max}}{Z} \quad \text{or equally} \quad I_{\text{rms}} = \frac{V_{\text{rms}}}{Z}$$

Thus

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{\sqrt{R^2 + (X_L - X_C)^2}} \quad \text{where } X_L = \omega L$$



$$X_C = \frac{1}{\omega C}$$

Thus, if the parameters are varied (perhaps by varying ω), the denominator will change.

The maximum I (minimum Z) occurs when $X_L = X_C$,

$$\text{ie } \omega L = \frac{1}{\omega C} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

↑ resonance frequency

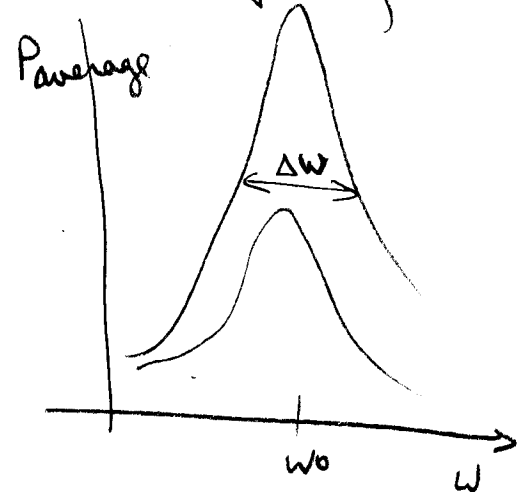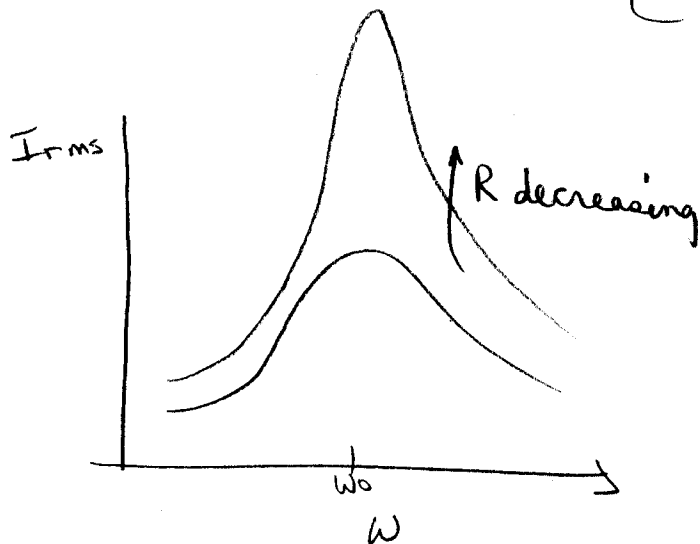

$\Delta\omega$ = full width at $\frac{1}{2}$ maximum.

Define $Q_0 = \frac{\omega}{\Delta\omega}$ = quality factor.

In terms of ω_0 :

$$\begin{aligned}
 P_{\text{average}} &= I_{\text{rms}}^2 R = \frac{V_{\text{rms}}^2 R}{(R^2 + (X_L - X_C)^2)} \\
 &= \frac{V_{\text{rms}}^2 R}{R^2 + (\omega L - \frac{1}{\omega C})^2} = \frac{V_{\text{rms}}^2 R}{R^2 + (\frac{L}{\omega})^2 (\omega^2 - \frac{1}{LC})^2} \\
 &= \frac{V_{\text{rms}}^2 R}{R^2 + (\frac{L}{\omega})^2 (\omega^2 - \omega_0^2)^2}
 \end{aligned}$$

Get max. power when $\omega = \omega_0$

High $Q_0 \Leftrightarrow$ narrow range

Low $Q_0 \Leftrightarrow$ wide range

ie a circuit will tend to resonate only over a narrow frequency range if Q_0 is high.

Example: radio tuner

Mechanical systems resonate in a similar fashion.

Example: A Resonating RLC circuit

$$R = 150 \Omega$$

$$L = 20 \text{ mH}$$

$$V_{\text{rms}} = 20 \text{ V}$$

$$\omega = 5000 \text{ sec}^{-1}$$

What is C for peak current at ω ?
What is the peak current?

$$\omega_0 = 5000 \text{ sec}^{-1} = \frac{1}{\sqrt{LC}}$$


$$\therefore C = \left(\frac{1}{\omega_0^2 L} \right) = \frac{1}{(5000)^2 \times 20 \times 10^{-3}} = \underline{2 \mu\text{F}}$$

$$I_{\text{max}} = \frac{20 \text{ V}}{\sqrt{(150)^2 + \underbrace{(X_L - X_C)^2}_{=0}}} = \frac{20}{150} = \underline{0.133 \text{ A}}$$

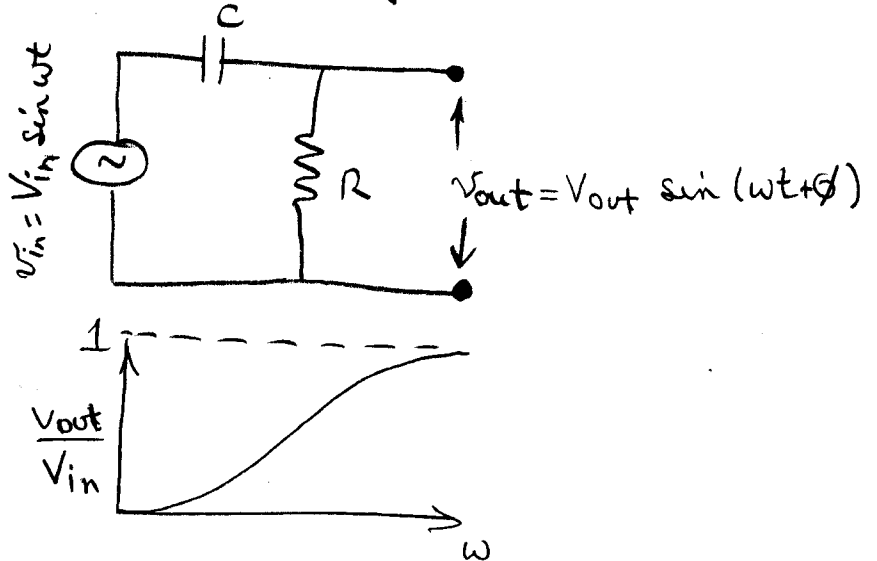33.8 Filter Circuits

Used to filter out unwanted frequencies.

High-pass filter
(passes high freq.,
filters low freq.)



From our results on RLC series circuits,

$$V_{in} = I_{max} Z = I_{max} \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$$


$$V_{out} = I_{max} R$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{R}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \rightarrow 0 \text{ as } \omega \rightarrow 0$$

Similarly, for a low-pass filter,

$$\frac{V_{out}}{V_{in}} = \frac{1/\omega C}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}}$$
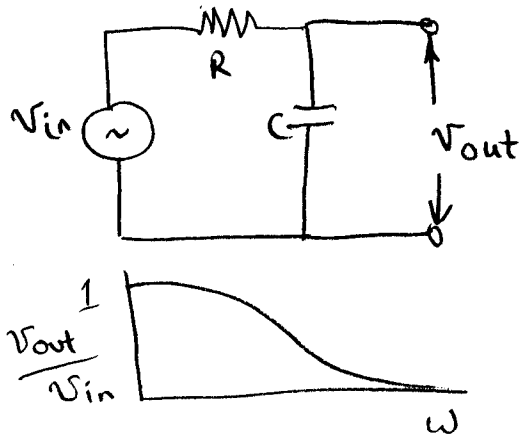
$$\rightarrow 0 \text{ as } \omega \rightarrow \infty$$



33.9 The Transformer and Power Transmission

Because of $i^2 R$ losses, it is desirable to keep i low in transmission lines. Since $P = iV$, the voltage must, therefore, be high.

At the user end, we need low voltage and high current for safety and efficiency.

Thus we need transformers.


Transformer

Faraday's law says $V = -N \frac{d\Phi}{dt} = -N \frac{d(B \cdot A)}{dt}$

where $\Phi = \text{magnetic flux} = \text{magnetic field} \times \text{area of loop}$.

A changing B field or area, i.e. a changing flux, induces a voltage (Emf).

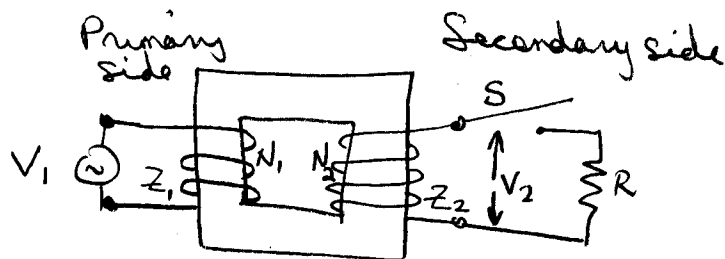We use wire loops to create a B field (solenoid) and an iron core to contain and direct the field:



$$V_1 = -N_1 \frac{d\Phi}{dt}, \quad V_2 = -N_2 \frac{d\Phi}{dt} \Rightarrow V_2 = \frac{N_2}{N_1} V_1$$

Thus, we can easily make a step-up or a step-down transformer by varying N_1 & N_2 .

If we close the switch, S , the induced voltage, V_2 , induces a current I_2 .

Since power in = power out (assuming no losses):

$$I_1 V_1 = I_2 V_2$$

$$\text{Now } I_2 = V_2 / R \quad \& \quad I_1 = V_1 / R_{eq}$$


where R_{eq} is the equivalent R as seen from the primary side (i.e. side 1).

$$\text{Since } V_1 = \frac{N_1}{N_2} V_2, \quad I_1 = \frac{N_1}{N_2} \frac{V_2}{R_{eq}} = \frac{N_1}{N_2} \frac{I_2 R}{R_{eq}}$$


\therefore From $I_1 V_1 = I_2 V_2$

$$\frac{N_1}{N_2} \frac{I_2 R}{R_{eq}} \cdot \frac{N_1}{N_2} V_2 = I_2 V_2$$
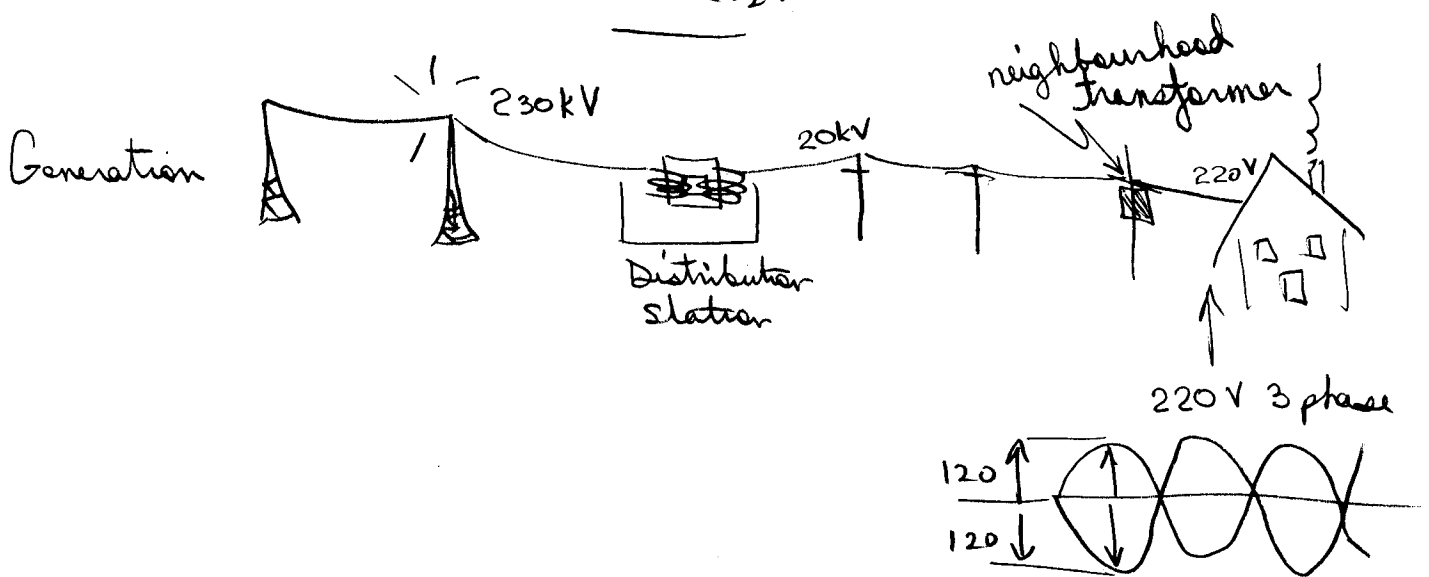
$$\Rightarrow R_{eq} = \left(\frac{N_1}{N_2} \right)^2 R$$



Example: A Step-Up Transformer

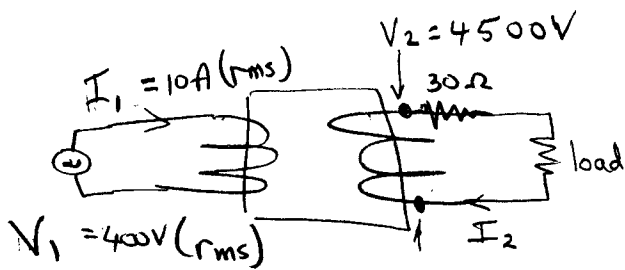

find % power lost.

$$I_2 = \frac{I_1 V_1}{V_2} = \frac{10 \times 400}{4500} = 0.89 \text{ A}$$

$$\begin{aligned} \therefore \text{Power in } R \text{ on secondary side} &= P_{\text{lost}} = I_2^2 R \\ &= (0.89)^2 (30) \\ &= 24 \text{ W} \end{aligned}$$

$$\text{Total power in} = I_1 V_1 = 4000 \text{ W.}$$

$$\therefore \% \text{ lost} = \frac{24}{4000} \times 100\% = 0.60\%$$

If a transformer had not been used:

$$I_2 = I_1 = 10 \text{ A}$$

$$\therefore P_{\text{lost}} = I_2^2 R = 3000 \text{ W.}$$

$$\therefore \% \text{ lost} = \frac{3000}{4000} \times 100\% = 75\%$$

If transmission line is cooled so that $30 \rightarrow 5 \Omega$, what is power lost if $I_2 = 0.89 \text{ A}$?

$$P_{\text{lost}} = (0.89)^2 (5) = 4.0 \text{ W,}$$

showing the advantage of cooling.

Cooling is costly, however.